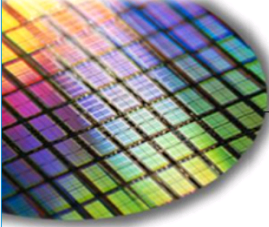


Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)



Amplifier Noise Principles for the Practical Engineer

Matt Duff
Applications Engineer – Instrumentation Amplifiers
Analog Devices, Inc.

copyright 2009



00:00:22 / 00:52:29

Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)



Outline

- ◆ **Noise**
 - Extrinsic
 - Intrinsic
- ◆ **Three main sources of intrinsic noise**
 - Resistance
 - Amplifier
 - ◆ Voltage Noise
 - ◆ Current Noise
 - ADC
- ◆ **Why so many units?**
 - $nV/\sqrt{Hz}$, μV_{rms} , μV_{p-p}
 - Unit conversion
- ◆ **Noise Math & Shortcuts**
- ◆ **Tips**
 - Applying gain
 - Source resistance
 - Feedback resistance

2



00:01:03 / 00:52:29

Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Extrinsic Noise

- ◆ Noise coupling in from external sources
- ◆ Examples
 - RFI Coupling
 - Power Supply Noise
 - Ground loops
 - ◆ Digital circuitry
 - ◆ 50/60 Hz
- ◆ Not focus of this talk

4

ANALOG DEVICES

00:02:22 / 00:52:29

Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Types of Resistor noise

- ◆ Excess Noise
 - Depends on type:
 - ◆ Carbon composition = bad performance
 - ◆ Thick film = OK performance
 - ◆ Thin film, wirewound = good performance
 - Increases with applied voltage
 - 1/f characteristic
 - Can ignore if using good resistors
- ◆ Intrinsic thermal noise
 - Independent of type
 - Independent of voltage applied
 - White noise characteristic
 - Need to calculate in design

8

ANALOG DEVICES

00:06:29 / 00:52:29

Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Thermal noise of an ideal resistor

$$v_n = \sqrt{4k T R \Delta f}$$

— bandwidth

rms noise constant Temperature (in Kelvin) resistance

9

ANALOG DEVICES

00:07:24 / 00:52:29

Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Resistor noise shortcut

$1 \text{ k}\Omega \rightarrow 4 \text{ nV}/\sqrt{\text{Hz}}$

Noise scales as square root of resistance



- $4 \text{ k}\Omega \rightarrow (2)(4) \text{ nV}/\sqrt{\text{Hz}} = 8 \text{ nV}/\sqrt{\text{Hz}}$
- $9 \text{ k}\Omega \rightarrow (3)(4) \text{ nV}/\sqrt{\text{Hz}} = 12 \text{ nV}/\sqrt{\text{Hz}}$
- $16 \text{ k}\Omega \rightarrow (4)(4) \text{ nV}/\sqrt{\text{Hz}} = 16 \text{ nV}/\sqrt{\text{Hz}}$
- $100 \text{ k}\Omega \rightarrow (10)(4) \text{ nV}/\sqrt{\text{Hz}} = 40 \text{ nV}/\sqrt{\text{Hz}}$

10

ANALOG DEVICES

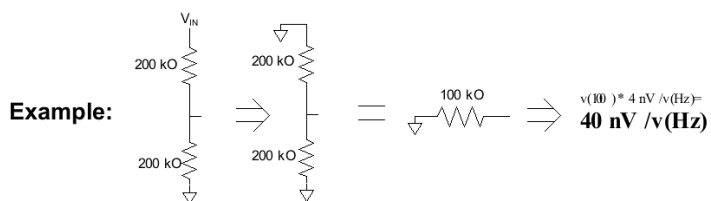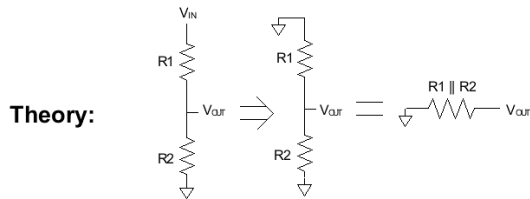00:08:13 / 00:52:29



Common Resistor Circuits: Resistor Divider



11

ANALOG
DEVICES

Common Resistor Circuits – Bridge

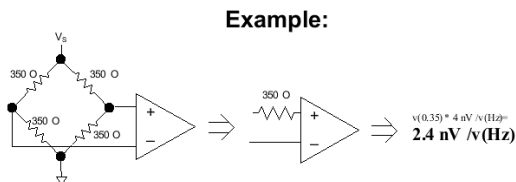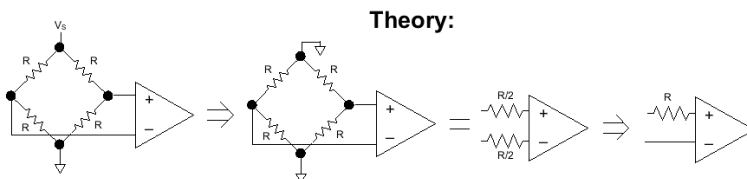

12


ANALOG
DEVICES

Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Amplifier Noise

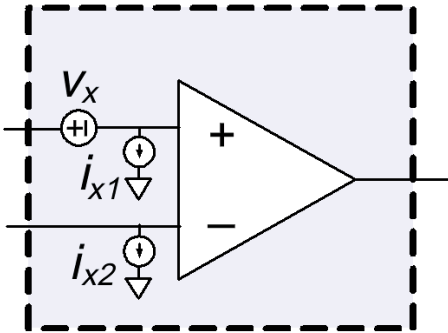

13

ANALOG DEVICES

00:11:38 / 00:52:29


Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Amplifier Voltage Noise: Referred to What?

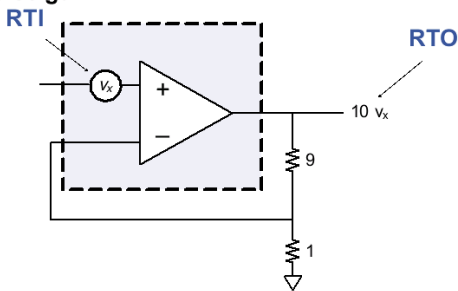- ◆ Options
 - Referred to Input (RTI)
 - Referred to Output (RTO)
- ◆ If not stated, referred to Input
- ◆ Multiply by "noise gain"



15

ANALOG DEVICES

00:13:04 / 00:52:29


Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Instrumentation Amplifiers are Different

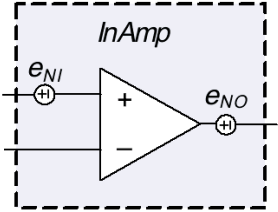- ◆ Op Amps
 - All noise dependent on gain
- ◆ In Amps
 - Some noise dependent on gain (e_{NI})
 - Some noise independent of gain (e_{NO})
- ◆ Total In Amp Noise, referred to input
 - $\sqrt{(e_{NI})^2 + (e_{NO}/G)^2}$



example from AD8221 datasheet:

Voltage Noise, 1 kHz	RTI Noise = $\sqrt{(e_{NI})^2 + (e_{NO}/G)^2}$	8	nV/ $\sqrt{\text{Hz}}$
Input Voltage Noise, e_{NI}	$V_{IN+}, V_{IN-}, V_{REF} = 0 \text{ V}$	75	nV/ $\sqrt{\text{Hz}}$
Output Voltage Noise, e_{NO}	$V_{IN+}, V_{IN-}, V_{REF} = 0 \text{ V}$		

16

ANALOG DEVICES


Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Amplifier Current Noise

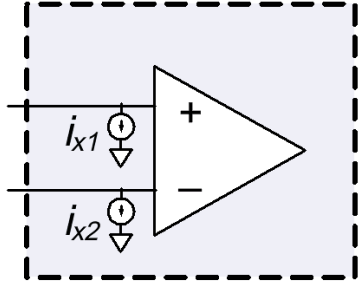- ◆ Units:
 - fA/ $\sqrt{\text{Hz}}$
 - pArms
 - pA p-p



example from AD8295 datasheet:


Current Noise	f = 1 kHz	40	fA/ $\sqrt{\text{Hz}}$
	f = 0.1 Hz to 10 Hz	6	pA p-p

17


ANALOG DEVICES

Amplifier Current Noise: Effect depends on resistance

◆ Source resistance

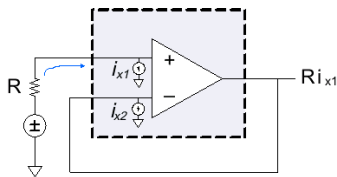

◆ Feedback network

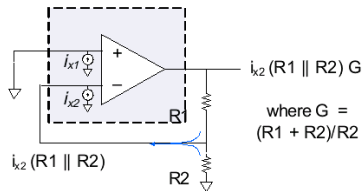

18



ADC Noise:

◆ Sometimes voltage units provided:

Table 6. RMS Noise (nV) vs. Gain and Output Data Rate

Filter Word (Decimal)	Output Data Rate (Hz)	Settling Time (ms)	Gain of					
			1	8	16	32	64	128
1023	4.7	852.5	340	53	34	18	12	11
640	7.5	533	410	67	40	24	14	13
480	10	400	430	76	45	28	16	15

◆ But most of the time, signal to noise ratio (SNR)

• With distortion: SINAD

Signal-to-Noise Ratio, SNR	$f_m = 20 \text{ kHz}, V_{NR} = 4.096 \text{ V, internal reference}$	87.0	88.5	dB
	$f_m = 20 \text{ kHz}, V_{NR} = 5.0 \text{ V, external reference}$	89.0	90.0	dB

◆ In emergency use ideal equation

- $SNR = 6.02 * \text{Bits} + 1.76$
- Gives better performance than reality

19



Network Recording Player - Kursor

File View Info Help


Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

ADC Noise – Converting SNR to μV_{rms}

Conversion Equation:

$$\frac{\text{Full Scale Voltage in } \mu V_{rms}}{10^{\frac{SNR}{20}}} = \text{ADC noise in } \mu V_{rms}$$

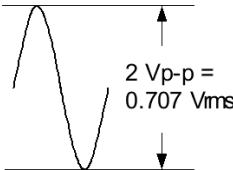Key Point: Use RMS value for full scale range!



Example:

- 2 V ADC input range
- 69 dB SNR

$$\frac{(2 \times 10^6 \mu V)(0.5)(.707)}{10^{\frac{69}{20}}} = 251 \mu V_{rms}$$

20

ANALOG DEVICES

00:19:05 / 00:52:29


Network Recording Player - Kursor

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Peak to Peak and RMS noise

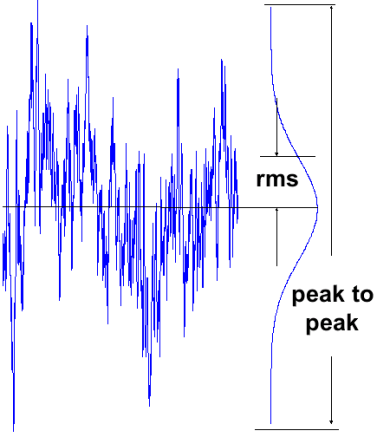- ◆ **Peak to peak noise**
 - Distance from min and max points on waveform
 - Depends on only two points
 - Less accurate
 - Variable
 - Measure longer -> bigger result
 - Easy to compute
 - Max - Min
- ◆ **RMS noise**
 - One standard deviation
 - (mean is zero)
 - Depends on all points
 - More accurate
 - Repeatable
 - Measure longer -> more accurate result
 - Lengthy to compute



$$\sqrt{\frac{x_1^2 + x_2^2 + \dots + x_n^2}{n}}$$

22

ANALOG DEVICES

00:19:52 / 00:52:29

Network Recording Player - Kursor

File View Info Help

Meeting Number: 794 232 482 | Date: Wednesday, November 04, 2009 | Time: 10:05 AM, Local Time (GMT -05:00)

RMS and Peak to Peak: Dependent on Bandwidth

- When measuring:
 - Circuit bandwidth
 - Measurement instrument bandwidth
- When specifying
 - Bandwidth must be noted

AD8222 Noise (G=100)

NOISE
RTI
G = 100 to 1000

f = 0.1 Hz to 10 Hz	0.25	μV p-p

23

ANALOG DEVICES

00:23:37 / 00:52:29

Network Recording Player - Kursor

File View Info Help

Meeting Number: 794 232 482 | Date: Wednesday, November 04, 2009 | Time: 10:05 AM, Local Time (GMT -05:00)

Spectral Noise Density

Voltage Noise Density | f = 1 kHz | 40 | nV/√Hz

Voltage Noise | f = 0.1 Hz to 10 Hz | 2.2 | μV p-p

- Frequency Domain
 - Noise density at specific frequency
- Units
 - nV/√Hz
 - fA/√Hz
- Includes many, many points
 - Datasheet figure has lots of averaging

AD8295


24

ANALOG DEVICES

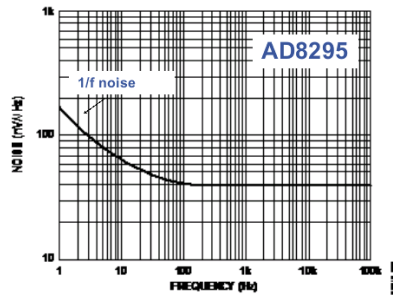00:25:17 / 00:52:29

Spectral Noise Density – 1/f corner

- ◆ **1/f noise**
 - Noise density increases at low frequencies
- ◆ **White noise**
 - Noise density flat at high frequencies
- ◆ **1/f corner**
 - Where 1/f noise and white noise trendlines intersect



25




nV/√(Hz) -> μVrms: theory

◆ Theoretical Equation

$$Noise_{RMS} = \sqrt{\int_{f_{LOW}}^{f_{HIGH}} (SD_f)^2 df}$$

◆ Where

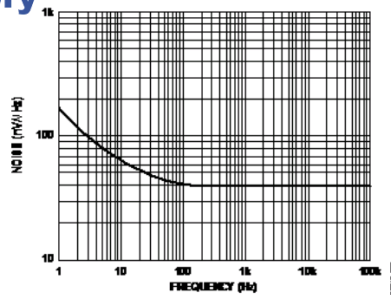- SD_f : spectral density at frequency f
- f_{LOW} : low frequency cutoff
- f_{HIGH} : high frequency cutoff



27




Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 | Date: Wednesday, November 04, 2009 | Time: 10:05 AM, Local Time (GMT -05:00)

nV/ $\sqrt{\text{Hz}}$ -> μV_{rms} shortcut

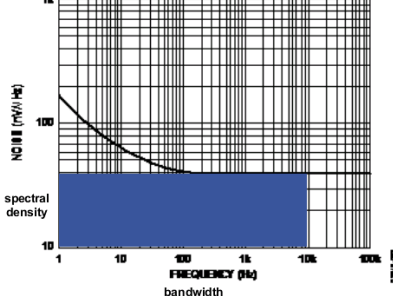- ◆ Assumption
 - Mostly white noise
 - ◆ 1/f corner << bandwidth



The graph shows Noise Density (nV/ $\sqrt{\text{Hz}}$) on the y-axis (log scale from 10 to 1k) versus Frequency (Hz) on the x-axis (log scale from 1 to 100k). A blue shaded region labeled 'spectral density' is shown under the noise curve. The curve starts at approximately 100 nV/ $\sqrt{\text{Hz}}$ at 1 Hz and decreases as frequency increases, following a 1/f relationship.

28

ANALOG DEVICES

00:32:51 / 00:52:29


Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 | Date: Wednesday, November 04, 2009 | Time: 10:05 AM, Local Time (GMT -05:00)

Equivalent Noise Bandwidth

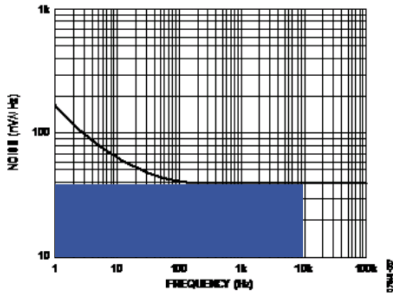- ◆ Equivalent Noise bandwidth for Butterworth filters
 - 1 pole: 1.57
 - 2 pole: 1.11
 - 3 pole: 1.05



The graph shows Noise Density (nV/ $\sqrt{\text{Hz}}$) on the y-axis (log scale from 10 to 1k) versus Frequency (Hz) on the x-axis (log scale from 1 to 100k). A blue shaded region is shown under the noise curve, representing the equivalent noise bandwidth.

29

ANALOG DEVICES

00:34:10 / 00:52:29

Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Equivalent Noise Bandwidth

- ◆ Equivalent Noise bandwidth for Butterworth filters
 - 1 pole: 1.57
 - 2 pole: 1.11
 - 3 pole: 1.05

29

ANALOG DEVICES

00:35:20 / 00:52:29

Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

$nV/\sqrt{Hz} \rightarrow \mu V_{rms}$

- ◆ Not mostly white noise?
 - $1/f$ corner near bandwidth
- ◆ Options
 - Use theoretical formula?
 - Use amplifier with low $1/f$ corner
 - Compare μV_{p-p} numbers
 - 0.1 to 10 Hz
 - Autozero/Chopper

Figure 16. Voltage Noise Density vs. Frequency

Figure 27. Voltage Noise Density

30

ANALOG DEVICES

00:38:07 / 00:52:29


Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

μVrms -> μVp-p

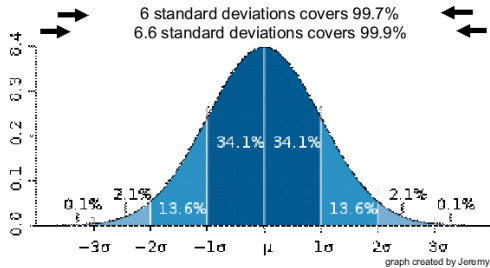- ◆ To get peak to peak noise
 - In theory: peak to peak noise infinite
 - In practice: multiply rms by 6
 - ◆ Multiplier of '6' is rule of thumb: 99.73% of points
- ◆ Examples
 - 1 μVrms * 6 ≈ 6 μVp-p
 - 1 μVrms * 6.6 ≈ 6.6 μVp-p



6 standard deviations covers 99.7%
6.6 standard deviations covers 99.9%

0.1% 2.1% 13.6% 34.1% 34.1% 13.6% 2.1% 0.1%

-3σ -2σ -1σ μ 1σ 2σ 3σ

graph created by Jeremy Kemp

31

ANALOG DEVICES

00:41:12 / 00:52:29



Network Recording Player - Kusior

File View Info Help


Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Noise Math


- ◆ Addition
 - Noise adds as sum of squares
- ◆ Multiplication
 - Gain and attenuation work just like normal signals

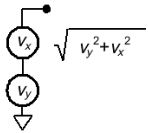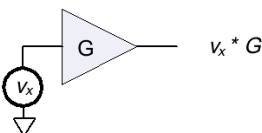Example

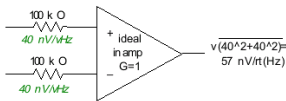

Example

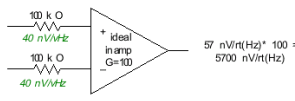

33

ANALOG DEVICES

00:43:10 / 00:52:29

Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Noise shortcuts

- ◆ 1 k Ω resistor $\rightarrow$ 4 nV/ $\sqrt{\text{Hz}}$
- ◆ When adding noise sources, larger sources dominate
 - Sum of squares addition
 - Ignore signals $< 1/5^{\text{th}}$ largest signal
- ◆ If first stage gain is large
 - Later stages typically have little effect

34

ANALOG DEVICES

00:43:24 / 00:52:29

Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Noise Tip #1: Apply Gain Early

- ◆ Noise adds as sum of squares

poor noise performance

$G=2$ $G=5$

good noise performance

$G=10$ $G=1$

36

ANALOG DEVICES

00:45:07 / 00:52:29


Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Noise Tip #2: Watch out for source impedance

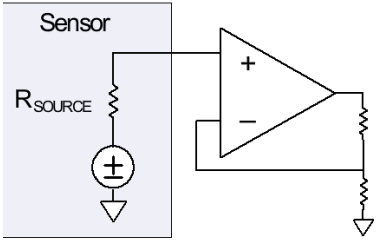- ◆ Source Resistance adds noise
- ◆ Current noise calculation



37

ANALOG DEVICES

00:45:34 / 00:52:29


Network Recording Player - Kusior

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Source impedance example


- ◆ Given the following sensor:

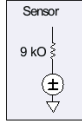

Sensor Noise :
 $v_9 \times 4 \text{ nV}/\sqrt{\text{Hz}}$
 $= 12 \text{ nV}/\sqrt{\text{Hz}}$

- ◆ Which op amp is better?

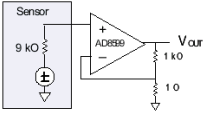
Ultralow Distortion, Ultralow Noise Op Amp
FEATURES
 $1.1 \text{ nV}/\sqrt{\text{Hz}}$
 $2.3 \text{ pA}/\sqrt{\text{Hz}} \times 9 \text{ k}\Omega = 20.7 \text{ nV}/\sqrt{\text{Hz}}$



Noise contributors (RTI):

Sensor noise	$= 4 \times v_9 =$	12
Amp Voltage noise	$=$	1.1
Amp Current noise	$= 2.3 \times 9 =$	20.7
Total Noise		$= v(12^2 + 1.1^2 + 20.7^2) =$
		24 nV/rt(Hz)

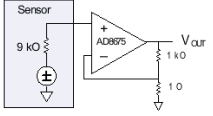36 V Precision, 2.8 nV/√Hz Rail-to-Rail Output Op Amp
FEATURES
 $2.8 \text{ nV}/\sqrt{\text{Hz}}$
 $0.3 \text{ pA}/\sqrt{\text{Hz}} \times 9 \text{ k}\Omega = 2.7 \text{ nV}/\sqrt{\text{Hz}}$



Noise contributors (RTI):

Sensor noise	$= 4 \times v_9 =$	12
Amp Voltage noise	$=$	2.8
Amp Current noise	$= 0.3 \times 9 =$	2.7
Total Noise		$= v(12^2 + 2.8^2 + 2.7^2) =$
		12.3 nV/rt(Hz)

38

ANALOG DEVICES

00:48:35 / 00:52:29

Network Recording Player - Kursor

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Noise Tip #3: Watch out for feedback resistors

- ◆ **Rf acts like voltage source at output**
- ◆ **Rg acts like inverting configuration voltage source**

Noise model of noninverting configuration

39

ANALOG DEVICES

00:49:49 / 00:52:29

Network Recording Player - Kursor

File View Info Help

Meeting Number: 794 232 482 Date: Wednesday, November 04, 2009 Time: 10:05 AM, Local Time (GMT -05:00)

Summary

- ◆ **Noise**
 - Extrinsic
 - Intrinsic
- ◆ **Three main sources of intrinsic noise**
 - Resistance
 - Amplifier
 - ◆ Voltage Noise
 - ◆ Current Noise
 - ADC
- ◆ **Why so many units?**
 - RMS noise, peak to peak noise, spectral density
 - How to convert between units
- ◆ **Noise Math & Shortcuts**
- ◆ **Tips**
 - Gain Early
 - Source Impedance
 - Feedback resistors

40

ANALOG DEVICES

00:50:46 / 00:52:29